
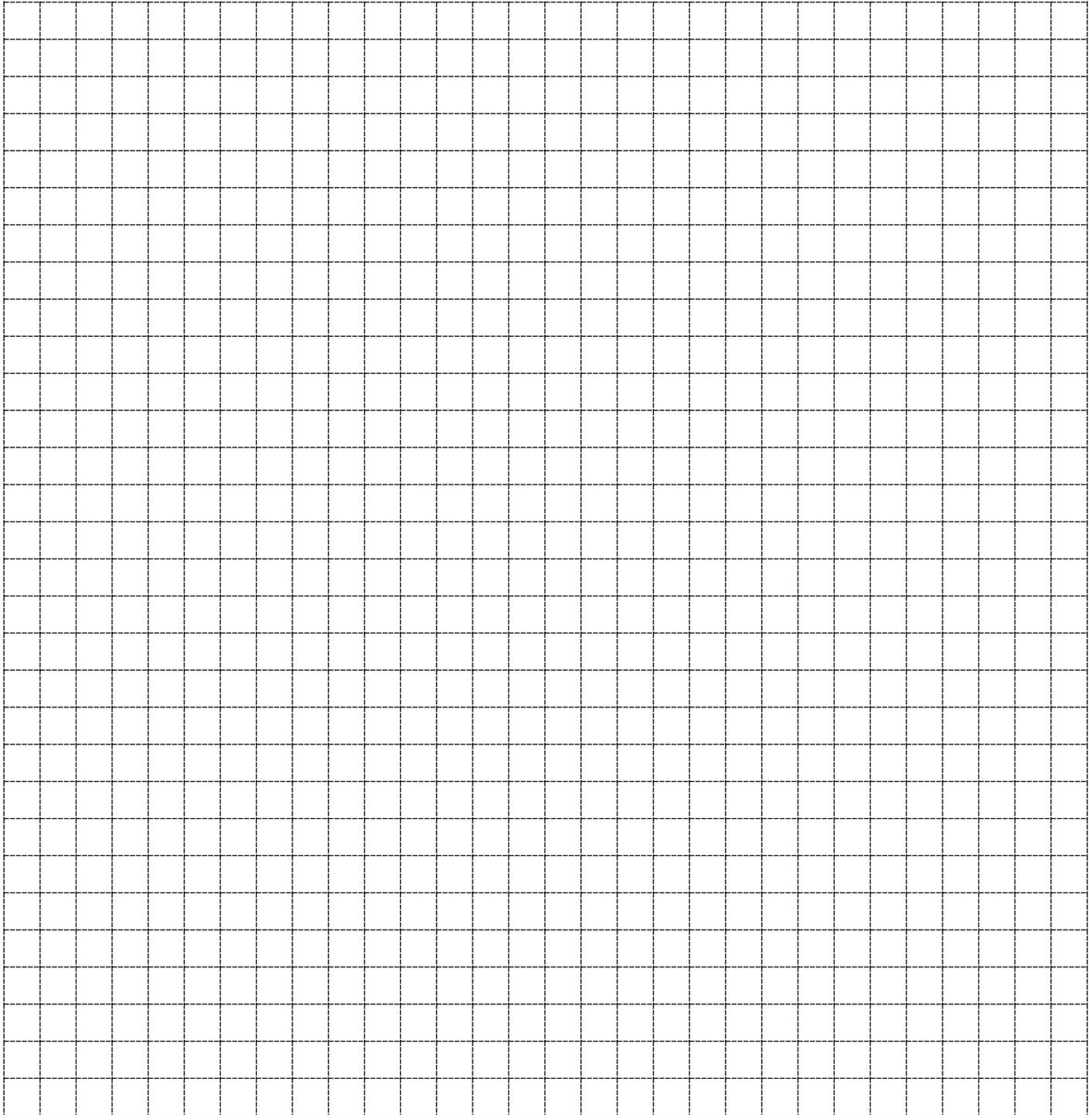


$U(\text{V})$	0	2	4	6	8	10
$I(\text{mA})$						
$U_{1k}(\text{V})$						
$U_{3k}(\text{V})$						

*table 1*

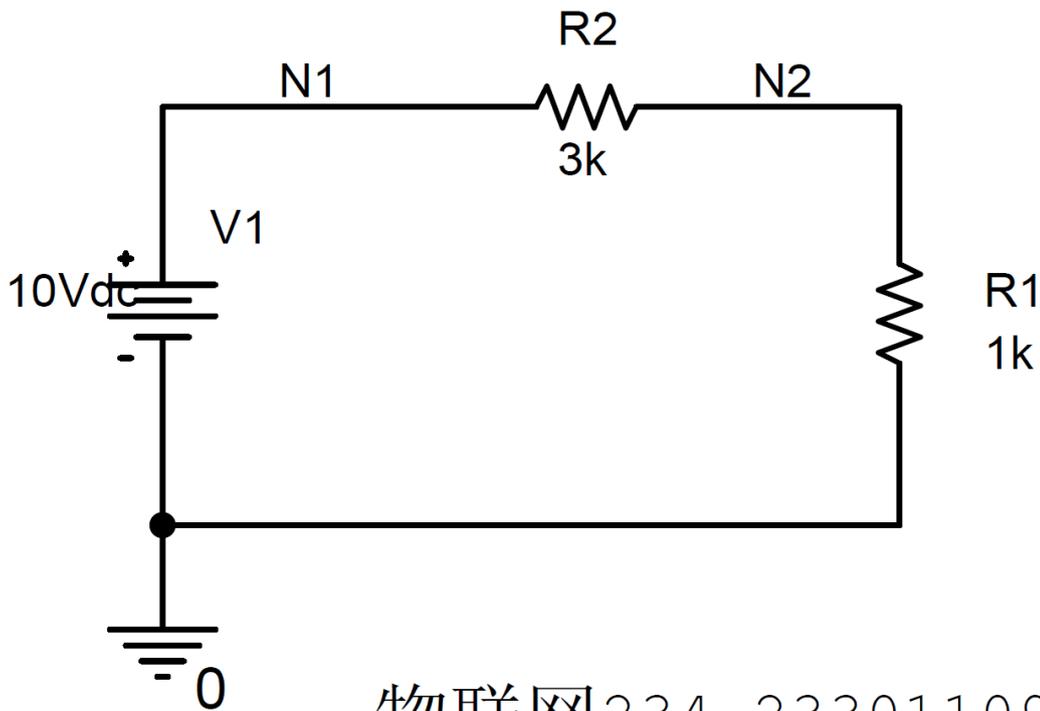


*graph 1*



物联网234\_2330110900\_张顾皓

fig 1-1

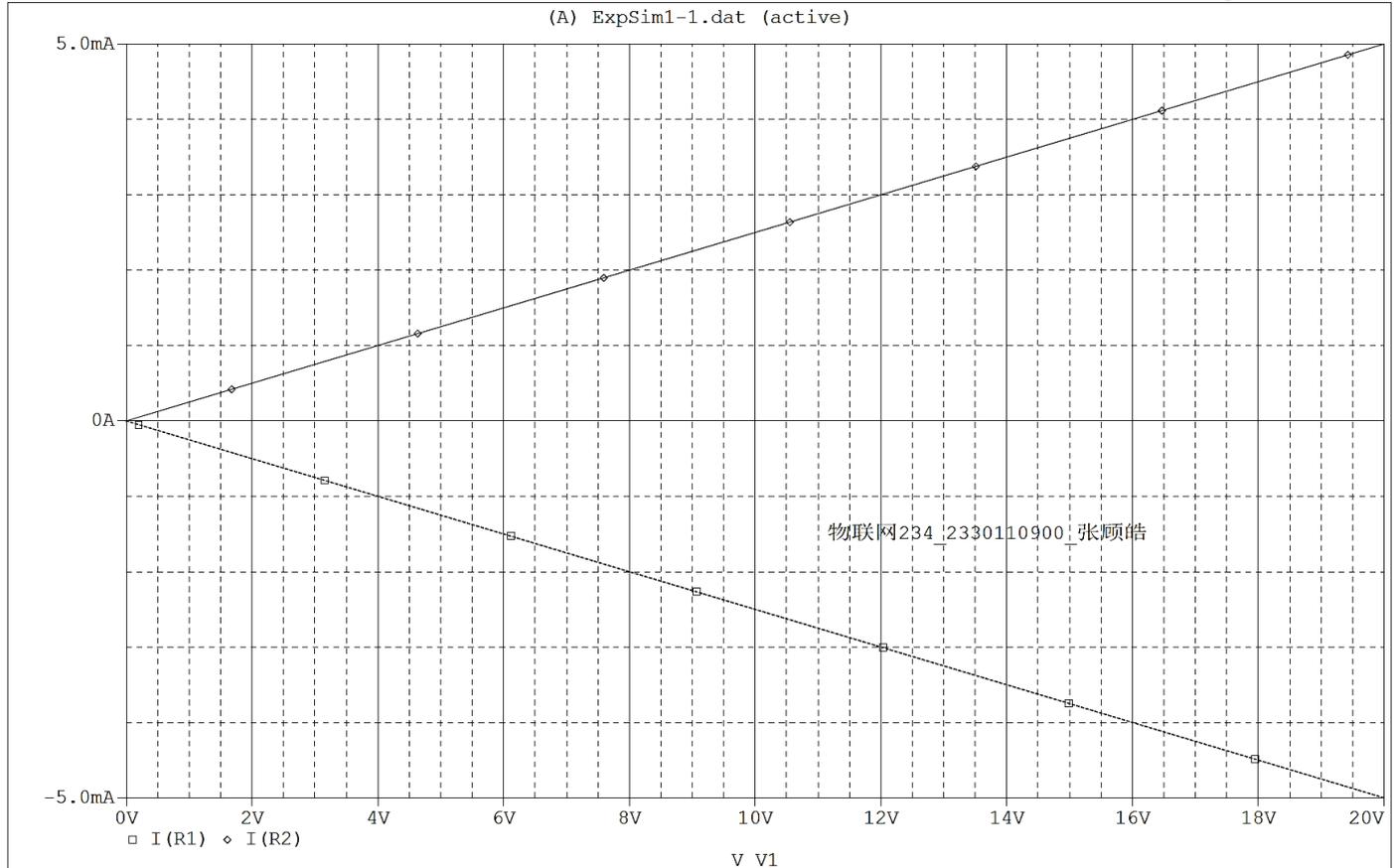\*\* Profile: "SCHEMATIC1-ExpSim1-1" [ F:\Projects\AnalogCircuit\CircuitExp1\1-1\CircuitExp1-1-PSpiceFiles\SCHEMA...  
 Date/Time run: 09/13/24 11:29:24 Temperature: 27.0



Date: September 13, 2024

Page 1

Time: 11:32:08

fig 1-2


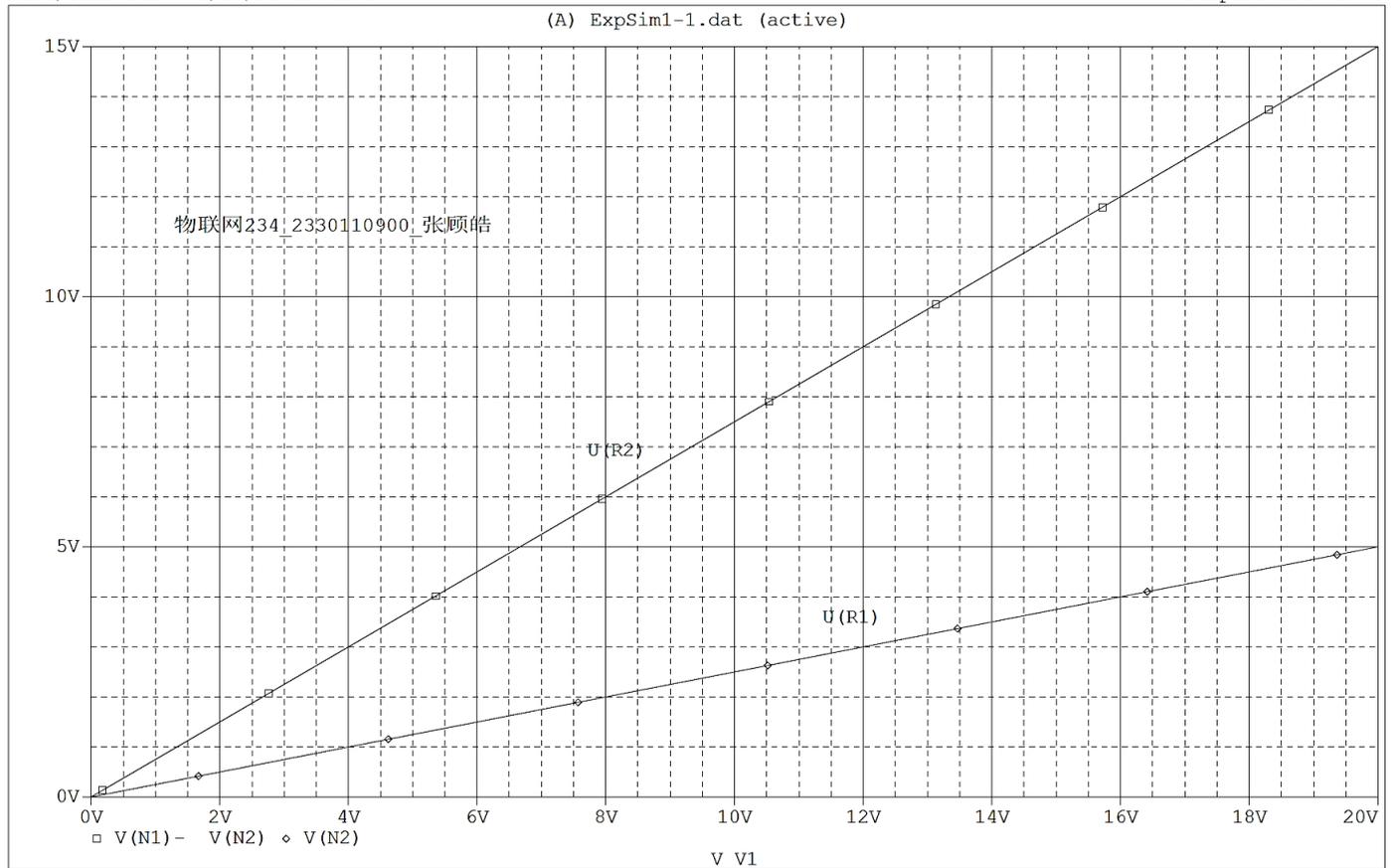



fig 1-3

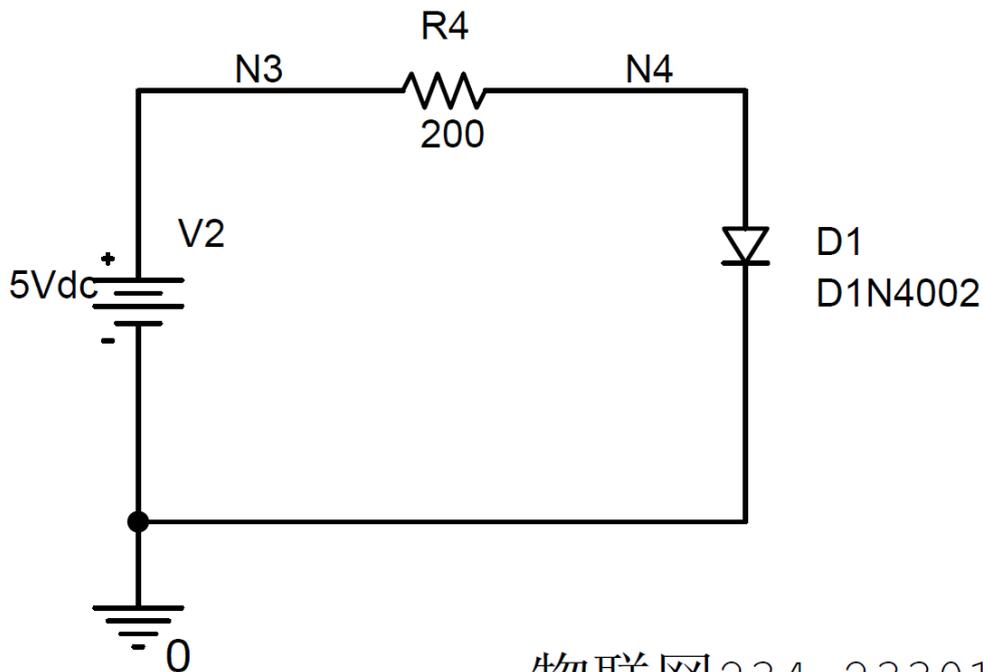

物联网234\_2330110900\_张顾皓

fig 2-1

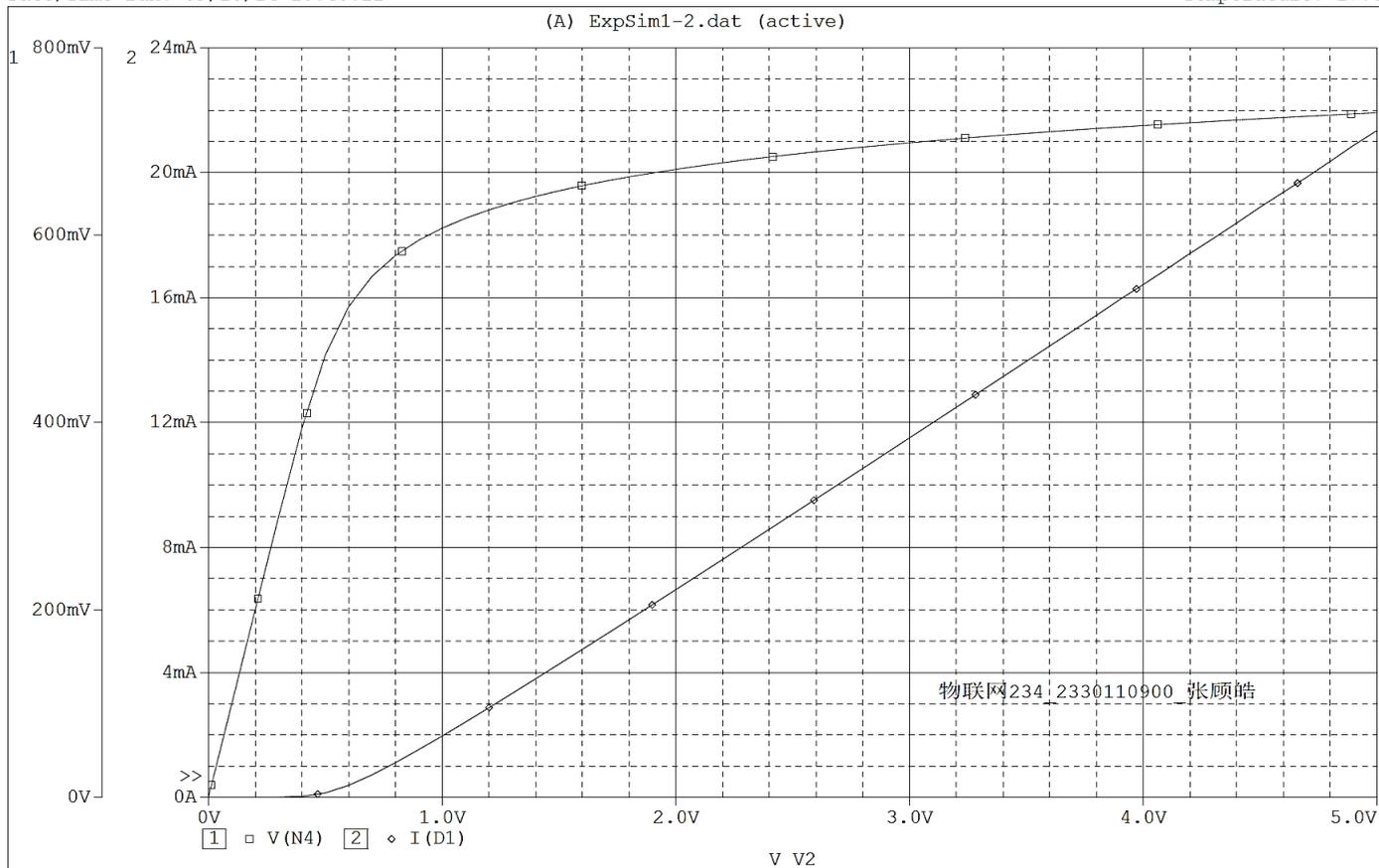\*\* Profile: "SCHEMATIC1-ExpSim1-2" [ F:\Projects\AnalogCircuit\CircuitExp1\1-2\CircuitExp1-2-PSpiceFiles\SCHEMA...  
 Date/Time run: 09/20/24 10:40:11 Temperature: 27.0



Date: September 20, 2024

Page 1

Time: 10:42:07

fig 2-2